

University of Information Technology & Sciences (UITs)
Faculty of Science and Engineering
Department of Computer Science and Engineering
Program: B.Sc. in CSE
Mid Term Examination, Spring 2024
Course Title: Electronic Device and Circuits
Course Code: EEE 251

Marks: 20

Time: 1(One) hour

(Answer all questions)

1. a) Describe the working principle of half and full wave rectifier [05]
with necessary circuit diagram.
- b) Draw the output waveshape with necessary explanation for the [05]
circuit shown in Figure 1


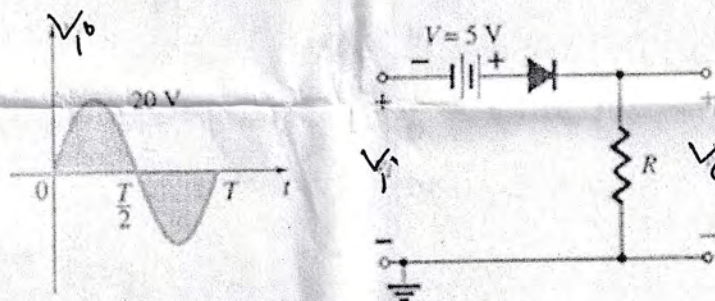


Figure 1 : Circuit for 1b

2. a) Find the V_o and draw the waveshape for the circuit shown in [05]
Figure 2 with detailed explanation. Take $V_i = 10V$

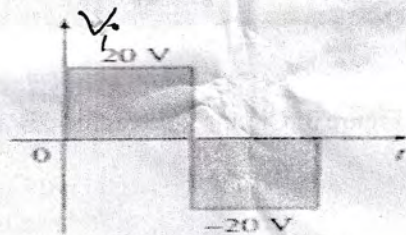

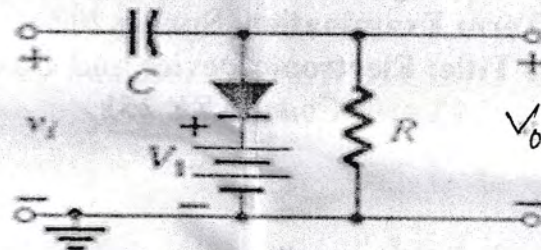


Figure 2: Circuit for question 2a

- b) Sketch the output waveshape with necessary explanation for [05]
the circuit shown in Figure 3.

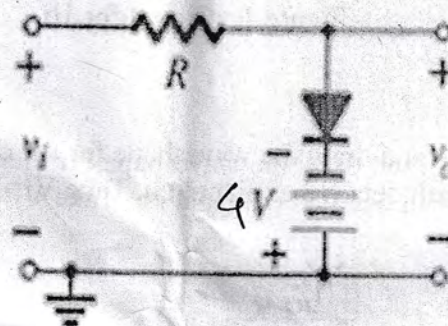
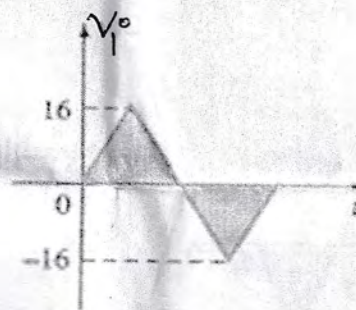


Figure 3: Circuit for question 2b