

University of Information Technology & Sciences (UITS)
Faculty of Science and Engineering
Department of Computer Science and Engineering
Program: B.Sc. in CSE
Term Final Examination, Autumn 2023
Course Title: Electronic Devices and Circuits
Course Code: EEE 251

Marks: 50

Time: 3 (three) Hours

(Answer all questions)

1. a) For the Zener diode network of figure 1, determine V_R , I_L , V_Z [05]

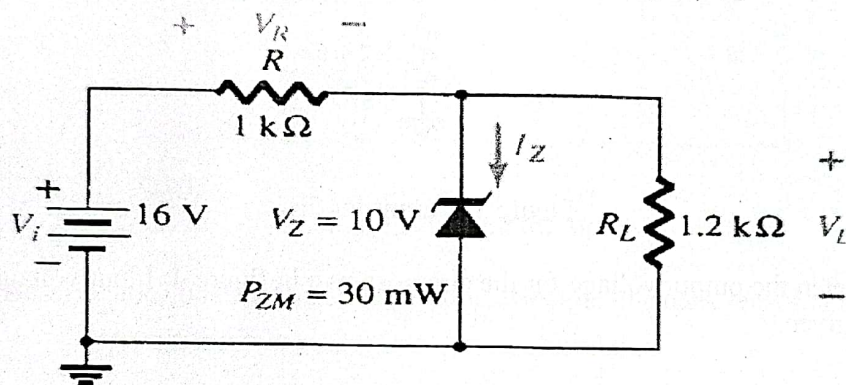


Figure 1: Circuit for 1a

- b) Describe the construction and the principle of a pnp transistor. [05]
2. a) Given the load line of figure 2 and the defined Q -point, determine the required values of V_{CC} , R_C , and R_B for a fixed-bias configuration. [05]

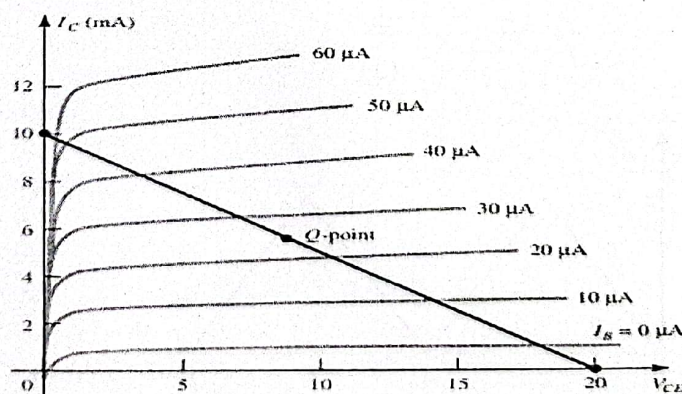


Figure 2: Circuit for 2a

- b) For the emitter-bias network of figure 3, determine I_B , I_C , V_{CE} , V_C , V_E , V_B and V_{BC} . [05]

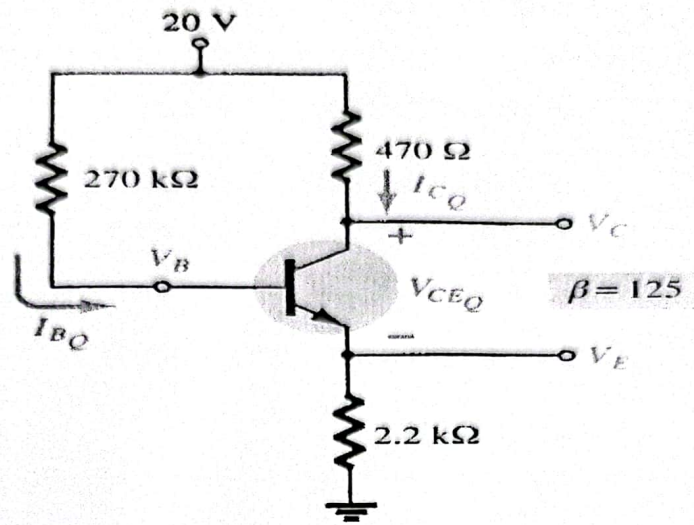


Figure 3: Circuit for 2b

3. a) Sketch the output voltage for the circuit shown in figure 4. Input voltage is given. [05]

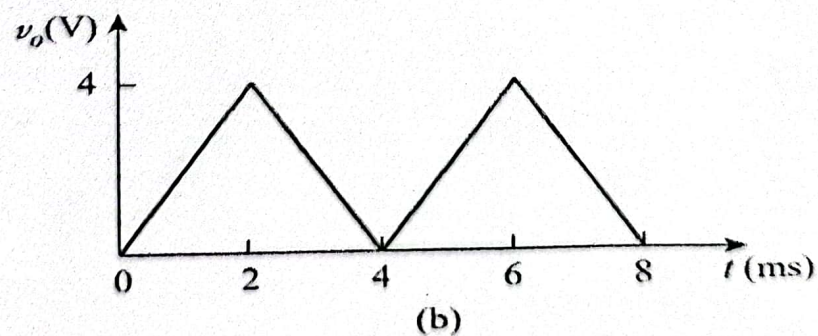
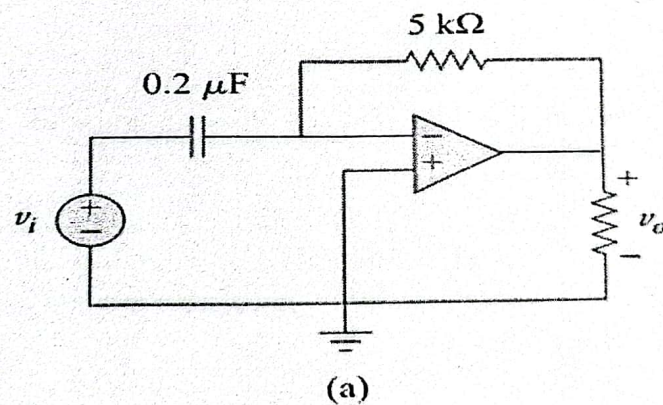


Figure 4: Circuit for 3a

- b) Explain the operation of a CMOS inverter with necessary circuit diagram. [05]
4. a) Explain the construction and characteristics of JFET. [05]
 b) Explain the basic construction and characteristics of Enhancement type MOSFET. [05]
5. a) Determine V_O and i_o in the op amp circuit shown in figure 5 [05]

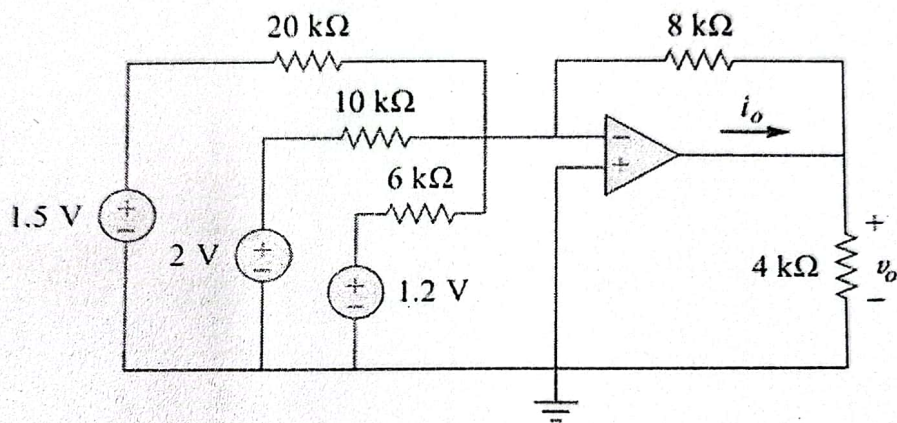


Figure 5: Circuit for 5a

- b) Describe the construction and operating principle of a dark sensor circuit. [05]