

University of Information Technology & Sciences (UITS)**Faculty of Science and Engineering****Department of Computer Science and Engineering****Program: B.Sc. in CSE****Term Final Examination, Autumn 2024****Course Title: Digital Logic Design****Course Code: CSE 215****Marks: 50****Time: 3(three) hours****(Answer all questions)**

1. a) Implement a Full Adder by using two 4x1 MUX. [03]
 b) Explain canonical form and convert the following to other canonical forms. [03]
 i. $F(A, B, C, D) = \sum (0, 2, 5, 6, 8, 9, 11, 14)$
 ii. $F(w, p, q) = \prod (0, 3, 7)$
 c) Convert the expression into sum of product and product of sum. [04]
 $F(A, B, C, D) = (AB + C)(B + C'D)$
2. a) Simplify the following Boolean function by using k-map [05]
 i. $F(A, B, C, D) = \sum (0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$
 ii. $F(w, x, y, z) = \prod (1, 3, 5, 7, 13, 15)$
 b) Simplify the Boolean function F using the don't-care conditions d, in i) sum [05]
 of minterm and ii) product of maxterm using K map.

$$F(A, B, C, D) = B'DE' + A'BE + B'C'E' + A'BC'D'$$

$$d(A, B, C, D) = BDE' + CD'E'$$

$$BCD' + A'BD + B'C'D' \quad / \quad BCD' + B'C'D'$$
3. a) Implement a full adder with two half adders and an OR gate. Also prove that [04]
 the complement of XOR is equal to XNOR.
 b) Construct a 5-to-32-line decoder with four 3-to-8-line decoders with enable [03]
 and one 2-to-4-line decoder and explain how it will work.
 c) An Encoder will produce a binary code equivalent to the minterm, which is [03]
 active High with enable. Design an 8 to 3 encoder with a truth table and
 circuit diagram.
4. a) The following three Boolean functions specify a combinational circuit: [05]

$$F_1(x, y, z) = (x' + y)z$$

$$F_2(x, y, z) = (y'z' + x'y + yz')$$

$$F_3(x, y, z) = (x + y)z$$
 Implement the circuit with a decoder constructed with OR gates. Use a block
 diagram for the decoder. Minimize the number of inputs in the external gates.
 b) State Flip Flop and construct T Flip Flop by using JK F/F. [05]

5. a) Design a sequential circuit from the following state diagram. (use JK F/F)

[10]

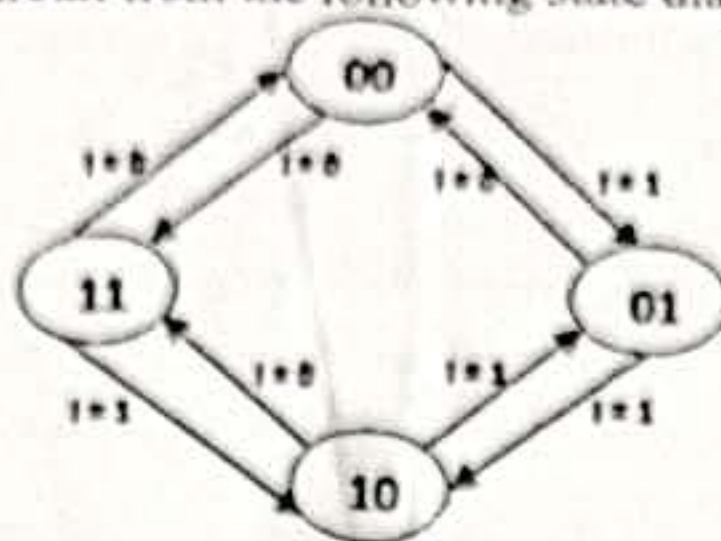


Figure 5(a)