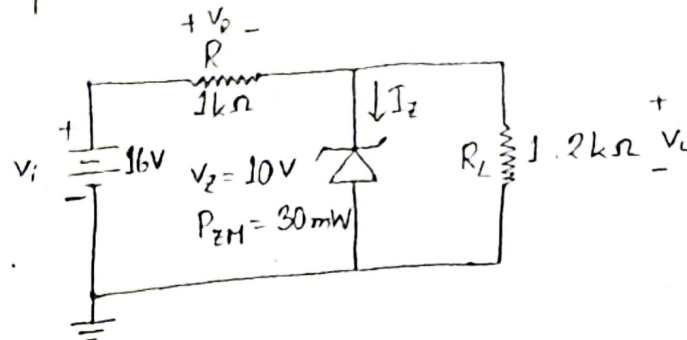


Zener Diode

Chapter: 02

Example: 2.26


- (a) For the Zener diode network of figure, determine V_L , V_R , I_Z and P_Z .
- (b) Repeat part (a) with $R_L = 3k\Omega$



Solution:-

$$(a) V_L = \frac{R_L}{R + R_L} \times V_i$$
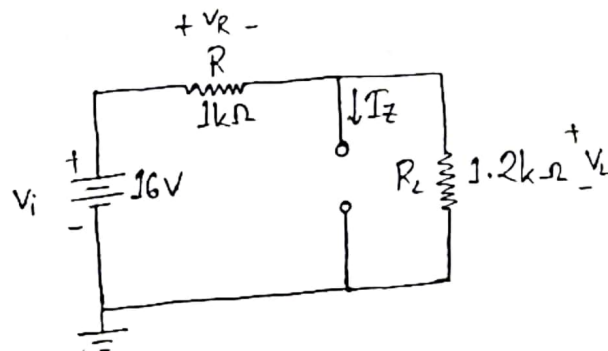
$$= \frac{1.2}{1 + 1.2} \times 16 = 8.73V$$




$$V_R = 16 - 8.73 = 7.27V$$

$$I_Z = 0mA$$

$$P_Z = 0mW$$

(b)

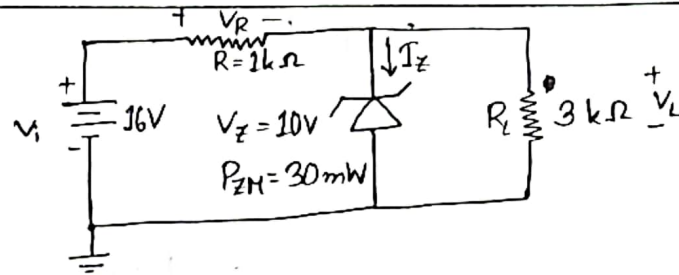

$$V_L = \frac{R_L}{R + R_L} \times V_i$$
$$= \frac{3}{1 + 3} \times 16$$
$$= 12V$$

$$V_L = 10V, V_Z = 10V$$


$$V_R = 16 - 10 = 6V$$

$$I_R = \frac{V_R}{R} = \frac{6}{1} = 6mA$$

$$I_L = \frac{V_L}{R_L} = \frac{10}{3} = 3.33mA$$

$$I_Z = 6 - 3.33 = 2.67mA$$

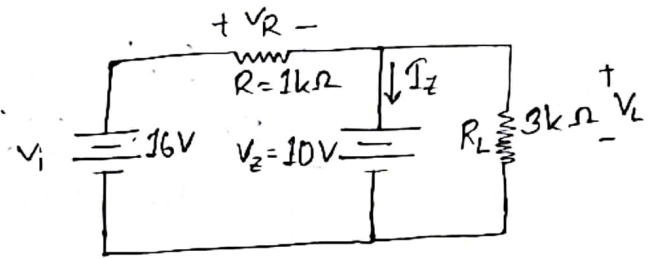
$$P_Z = V_Z I_Z = 10 \times 2.67 = 26.7mW$$



Example:

2.27

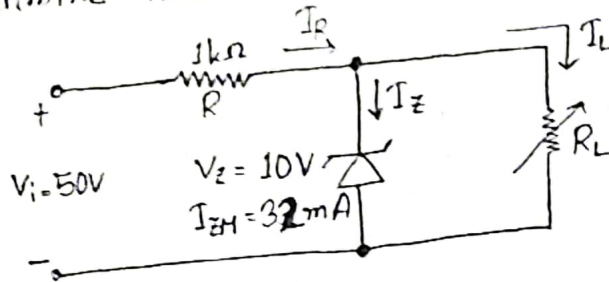- (a) For the network of figure, determine the range of R_L and I_L that will result in V_{RL} being maintained at 10V.
- (b) Determine the maximum wattage rating of the diode.



Solution:-

$$(a) V_L = V_Z = \frac{R_L}{R_L + R} \times V_i$$

$$\left| \begin{array}{l} R = 1k\Omega \\ = 1000\Omega \end{array} \right.$$

$$\Rightarrow 10 = \frac{R_L}{R_L + 1000} \times 50$$

$$\Rightarrow 10 = \frac{50R_L}{R_L + 1000}$$

$$\Rightarrow 10R_L + 10000 = 50R_L$$

$$\therefore R_{Lmin} = 250\Omega$$

$$V_R = 50V - 10V = 40V$$

$$I_R = \frac{V_R}{R} = \frac{40}{1000} = 0.04A = 40mA$$

$$I_{max} = \frac{10}{250} = 0.04A$$


$$I_{Lmin} = 40 - 32 = 8mA$$

$$R_{max} = \frac{10}{8} = 1.25k\Omega = 1250\Omega$$

$$\begin{aligned}
 (b) \quad P &= V_Z I_{ZM} \\
 &= 10V \times 32mA \\
 &= 320mW
 \end{aligned}$$

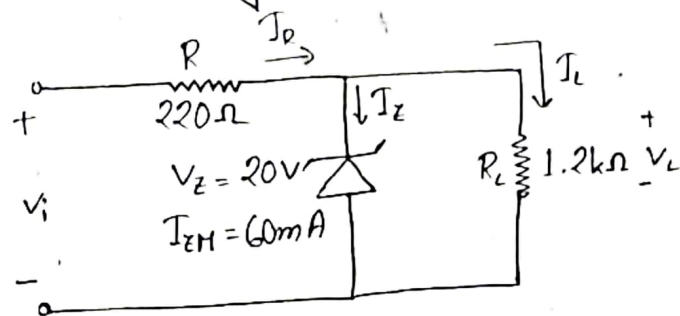Example:
2.28

Determine the range of values of V_i that will maintain the Zener diode of figure in the "on" state.



Solution:-

$$V_Z = \frac{R_L}{R_L + R} \times V_i$$

$$\Rightarrow 20 = \frac{1200}{1200 + 220} \times V_i$$

$$\therefore V_{i\min} = 23.67V$$

$$I_L = \frac{20}{1200} = 0.0167A = 16.67mA$$


$$I_R = 60 + I_L = 60 + 16.67 = 76.67mA$$

$$\begin{aligned}
 V_R &= 220 \times 76.67 = 16867.4mV \\
 &= 16.86V
 \end{aligned}$$

$$\begin{aligned}
 V_{i\max} &= (16.86 + 20)V \\
 &= 36.86V
 \end{aligned}$$

BJTChapter: 4Example:4.1

Determine the following for the fixed-bias configuration

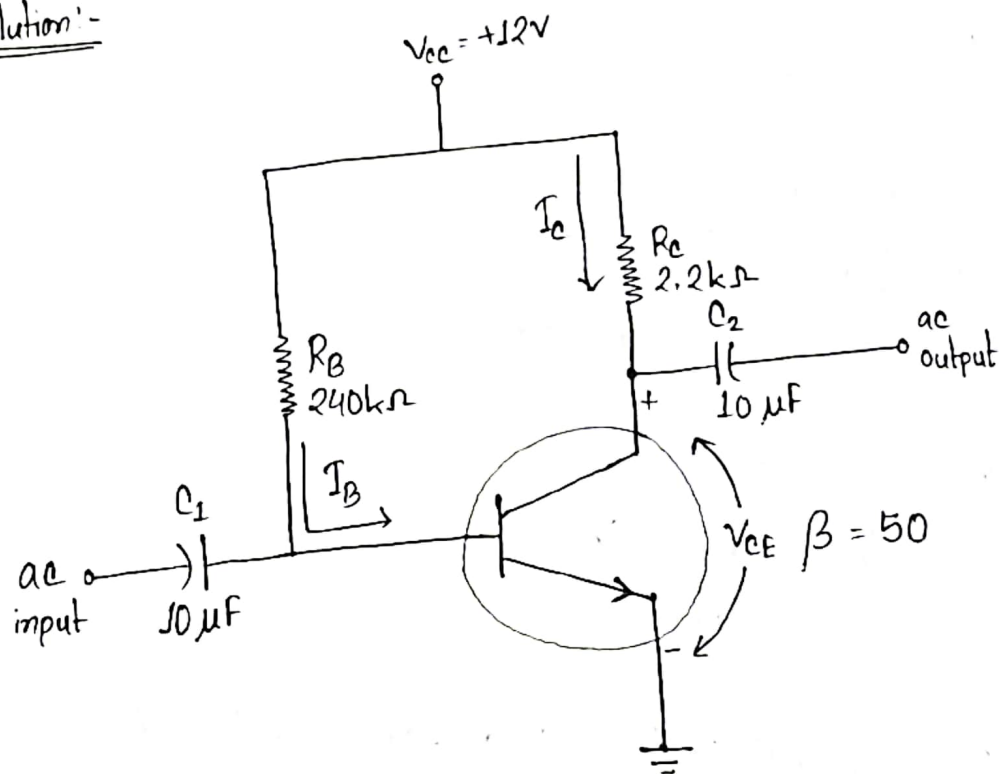(a) I_{BQ} and I_{CQ} (b) V_{CEQ} (c) V_B and V_C (d) V_{BE} Solution:-

Applying KVL at input side,

$$-V_{CC} + I_B R_B + V_{BE} = 0$$

$$\Rightarrow I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$\therefore I_B = \frac{12 - 0.7}{240} = 0.047 \text{ mA}$$

$$I_c = \beta I_B$$

$$= 50 \times 0.047 = 2.354 \text{ mA}$$

Applying KVL at output side,

$$-V_{cc} + I_c R_c + V_{ce} = 0$$

$$\Rightarrow V_{ce} = V_{cc} - I_c R_c$$

$$\therefore V_{ce} = 12 - (2.35 \times 2.2)$$

$$= 6.83 \text{ V}$$

$$V_{BE} = V_B - V_E$$

$$\Rightarrow V_B = V_{BE} + V_E$$

$$\therefore V_B = 0.7 + 0 = 0.7 \text{ V}$$

$$V_{ce} = V_c - V_E$$

$$\Rightarrow V_c = V_{ce} + V_E$$

$$\therefore V_c = 6.83 + 0 = 6.83 \text{ V}$$

$$V_{BC} = V_B - V_c$$

$$= (0.7 - 6.83) \text{ V}$$

$$= -6.13 \text{ V}$$

(a) $I_{BQ} = 0.047 \text{ mA}$ and $I_{CQ} = 2.35 \text{ mA}$

(b) $V_{CEQ} = 6.83 \text{ V}$


(c) $V_B = 0.7 \text{ V}$ and $V_c = 6.83 \text{ V}$

(d) $V_{BC} = -6.13 \text{ V}$

Example :

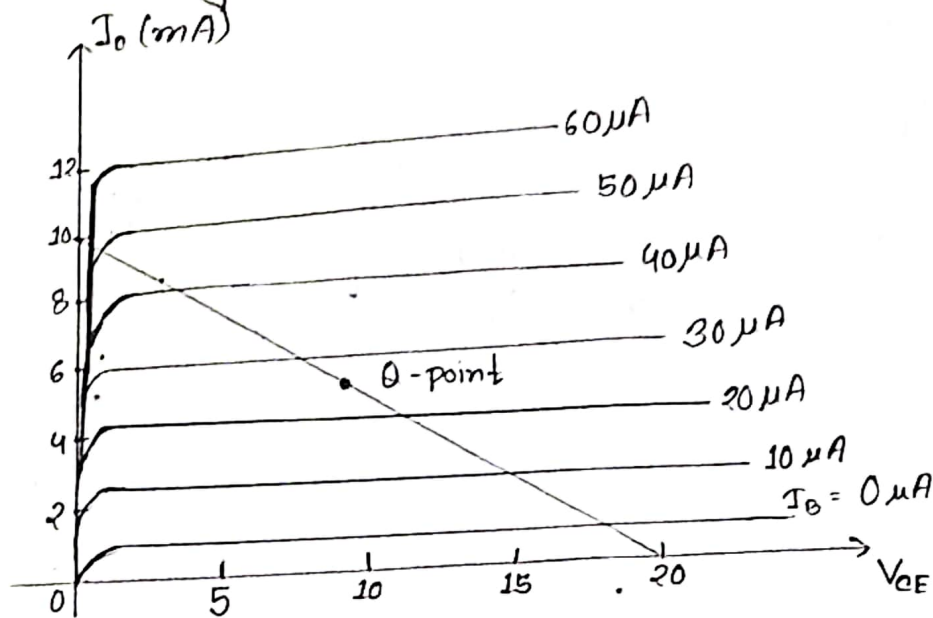4.3

Given the load line of figure and the defined Q-point, determine the required values of V_{CC} , R_C and R_B for a fixed-bias configuration.



Solution:-

$$I_B = 25 \mu A$$

$$\frac{V_{CC}}{R_C} = 10, \quad V_{CC} = 20$$

$$R_C = \frac{V_{CC}}{I_C} = \frac{20}{10} = 2 k\Omega$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$\Rightarrow R_B = \frac{V_{CC} - V_{BE}}{I_B}$$

$$\Rightarrow R_B = \frac{20 - 0.7}{25 \times 10^{-6}}$$


$$\therefore R_B = 772 k\Omega$$

Example:

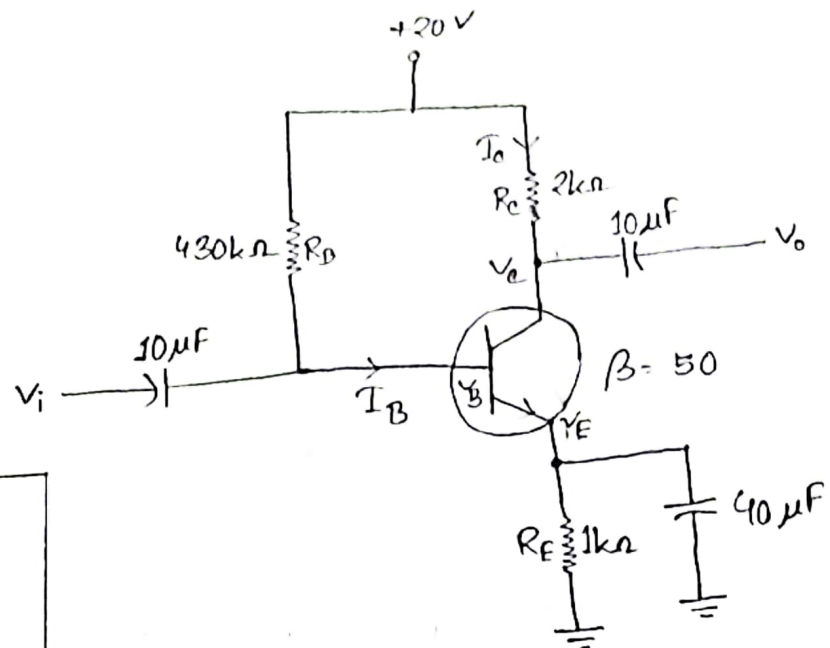4.4

For the emitter-bias network of figure, determine:

- I_B
- I_C
- V_{CE}
- V_o
- V_E
- V_B
- V_{BE}



$$I_E = I_B + I_C$$

$$I_E = I_C$$

$$I_C = \beta I_B$$

$$I_E = I_B (\beta + 1)$$

Solution:-

Applying KVL at input side,

$$-V_{CC} + I_B R_B + V_{BE} + I_E R_E = 0$$

$$\Rightarrow -V_{CC} + I_B R_B + V_{BE} + I_B (\beta + 1) R_E = 0$$

$$\Rightarrow I_B (R_B + (\beta + 1) R_E) = V_{CC} - V_{BE}$$

$$\Rightarrow I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E}$$

$$\Rightarrow I_B = \frac{20 - 0.7}{430 + (50 + 1) \cdot 1}$$

$$\therefore I_B = 0.04 \text{ mA}$$

$$I_e = \beta I_b = 50 \times 0.04 = 2 \text{ mA}$$

Applying KVL at output side,

$$-V_{CC} + I_e R_c + V_{CE} + I_e R_E = 0$$

$$\Rightarrow -V_{CC} + I_e R_c + V_{CE} + I_e R_E = 0$$

$$\Rightarrow I_e (R_c + R_E) = V_{CC} - V_{CE}$$

$$\Rightarrow V_{CE} = V_{CC} - I_e (R_c + R_E)$$

$$\Rightarrow V_{CE} = 20 - 2(2 + 1)$$

$$\therefore V_{CE} = 14 \text{ V}$$

$$V_c = V_{CC} - I_e R_c$$

$$= 20 - 2 \times 2 = 16 \text{ V}$$

$$V_{CE} = V_c - V_E$$

$$\Rightarrow V_E = V_c - V_{CE} = 16 - 14 = 2 \text{ V}$$

$$V_{BE} = V_B - V_E$$

$$\Rightarrow V_B = V_{BE} + V_E = 0.7 + 2 = 2.7 \text{ V}$$

$$V_{BC} = V_B - V_c$$

$$= 2.7 - 16 = -13.3 \text{ V}$$

a. $I_B = 0.04 \text{ mA}$

b. $I_c = 2 \text{ mA}$

c. $V_{CE} = 14 \text{ V}$

d. $V_c = 16 \text{ V}$



e. $V_E = 2 \text{ V}$

f. $V_B = 2.7 \text{ V}$

g. $V_{BC} = -13.3 \text{ V}$

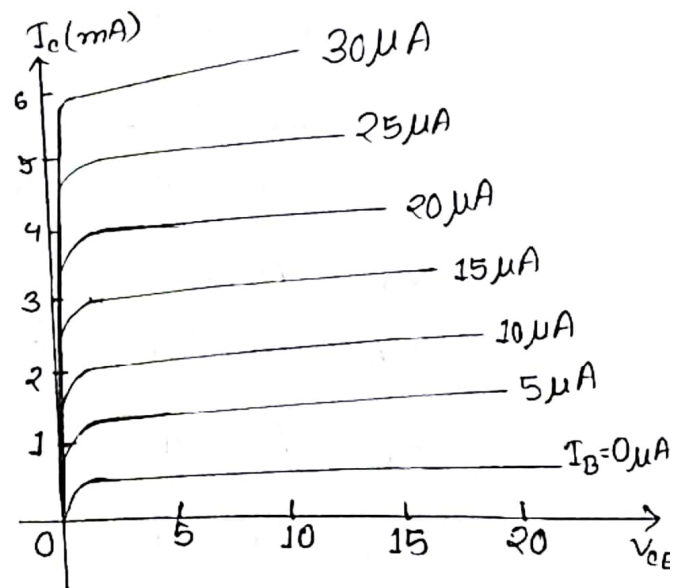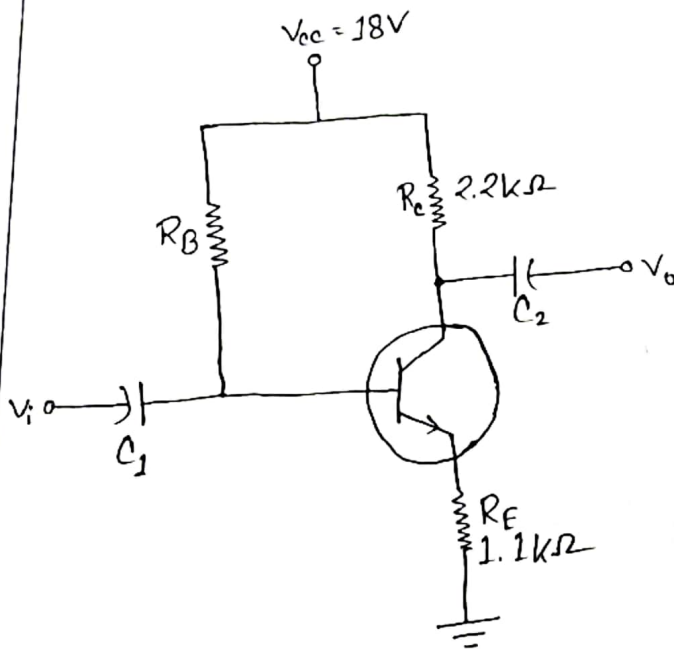Example:
4.7

- Draw the load line for the network of figure on the characteristics for the transistor appearing in figure.
- For a Q-point at the intersection of the load line with a base current of $15\mu A$, find the values of I_{CQ} and V_{CEQ} .
- Determine the dc beta at the Q-point.
- Using the beta for the network determined in part c, calculate the required value of R_B and suggest a possible standard value.




Solution:-

(a) Load Curve:

$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

When, $V_{CE} = 0$, $I_C = \frac{V_{CC}}{R_C + R_E} = \frac{18}{2.2 + 1.1} = 5.45 \text{ mA}$

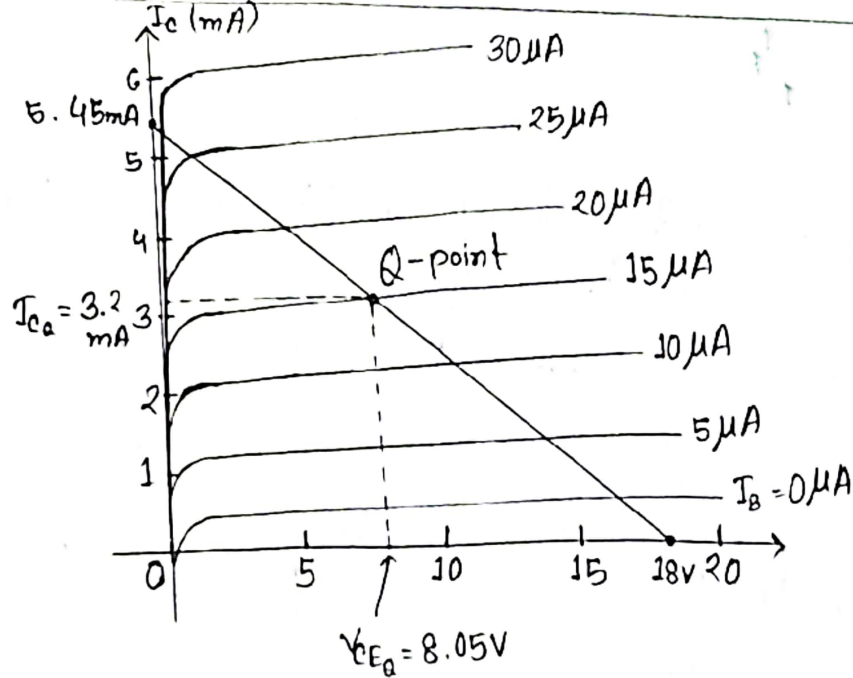When, $I_C = 0$, $V_{CC} = V_{CE} = 18 \text{ V}$



(b) From the characteristics,

$$I_{CQ} = 3.2 \text{ mA} ; V_{CEQ} = 8.05 \text{ V}$$

$$(c) \beta = \frac{I_{CQ}}{I_{BQ}} = \frac{3.2 \times 10^{-3}}{15 \times 10^{-6}} = 213$$

d) Applying KVL at input side,

$$-V_{CC} + I_B R_B + V_{BE} + I_E R_E = 0$$

$$\Rightarrow -V_{CC} + I_B R_B + V_{BE} + I_B (\beta + 1) R_E = 0$$

$$\Rightarrow I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E}$$

$$\Rightarrow R_B = \frac{V_{CC} - V_{BE} - (\beta + 1) R_E I_B}{I_B}$$


$$\therefore R_B = \frac{18 - 0.7 - (220 + 1) \times 1.1 \times 15 \times 10^{-3}}{15 \times 10^{-3}}$$

$$= 910.23 \text{ k}\Omega$$

Example:

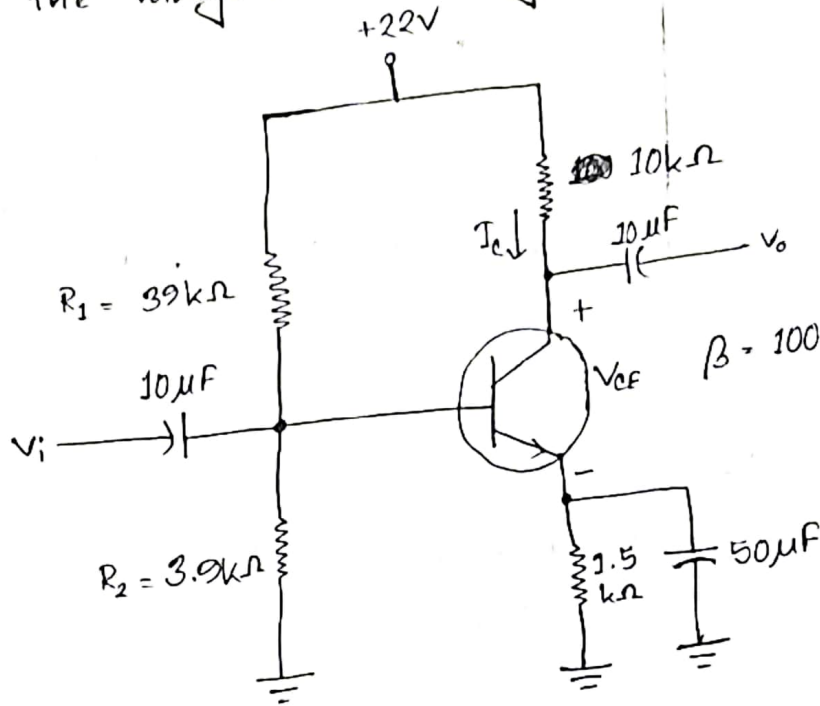4.8

Determine the dc bias voltage V_{CE} and the current I_C for the voltage-divider configuration of figure.



Solution:-

$$\begin{aligned} V_{th} &= \frac{R_2}{R_1 + R_2} \times V_{CC} \\ &= \frac{3.9}{39 + 3.9} \times 22 \\ &= 2V \end{aligned}$$

$$\begin{aligned} R_{th} &= R_1 \parallel R_2 = \frac{R_1 \times R_2}{R_1 + R_2} \\ &= \frac{39 \times 3.9}{39 + 3.9} = 3.54k\Omega \end{aligned}$$

Applying KVL at input side,

$$-V_{th} + I_B R_{th} + V_{BE} + I_E R_E = 0$$


$$\Rightarrow -V_{th} + I_B R_{th} + V_{BE} + I_B (\beta + 1) R_E = 0$$

$$\Rightarrow I_B = \frac{V_{th} - V_{BE}}{R_{th} + (\beta + 1) R_E}$$

$$\Rightarrow I_B = \frac{2 - 0.7}{3.54 + (100 + 1) 1.5}$$

$$\therefore I_B = 8.38 \mu A$$
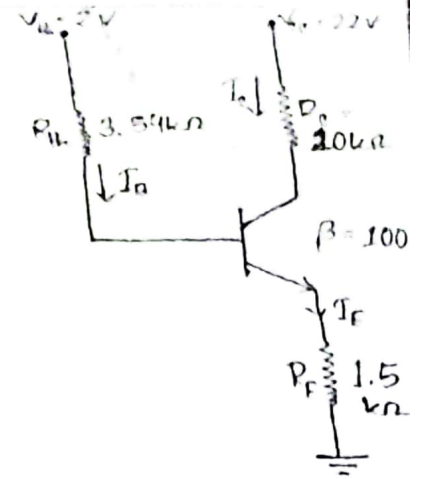
$$I_C = \beta I_B = 100 \times 8.38 = 838 \mu A$$
$$= 838 \times 10^{-3} \text{ mA}$$



Applying KVL at output side,

$$-V_{CC} + I_C R_C + V_{CE} + I_E R_E = 0$$

$$\Rightarrow -V_{CC} + I_C R_C + V_{CE} + I_C R_E = 0$$

$$\Rightarrow V_{CE} = V_{CC} - I_C (R_C + R_E)$$


$$\Rightarrow V_{CE} = 22 - 838 \times 10^{-3} (10 + 1.5)$$

$$\therefore V_{CE} = 12.36 \text{ V}$$


Example:

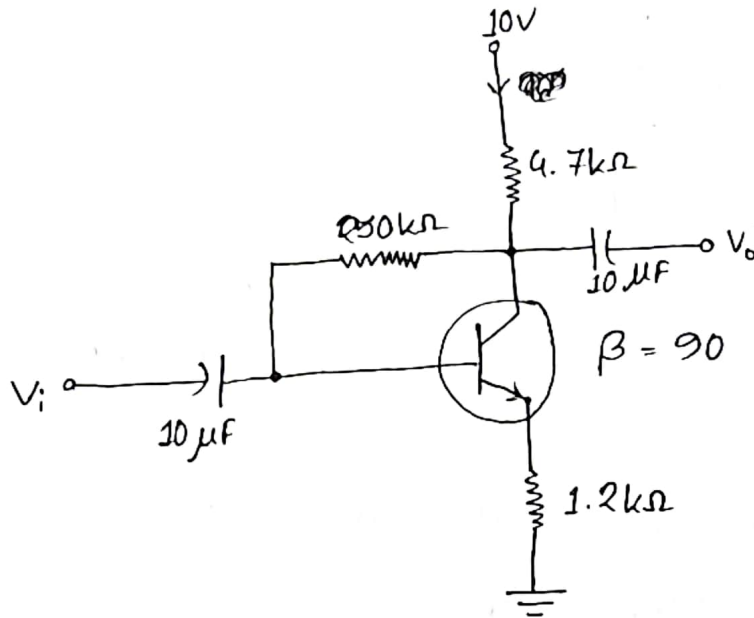4.12

Determine the quiescent levels of I_{CQ} and V_{CEQ} for the network of figure.



Solution:-

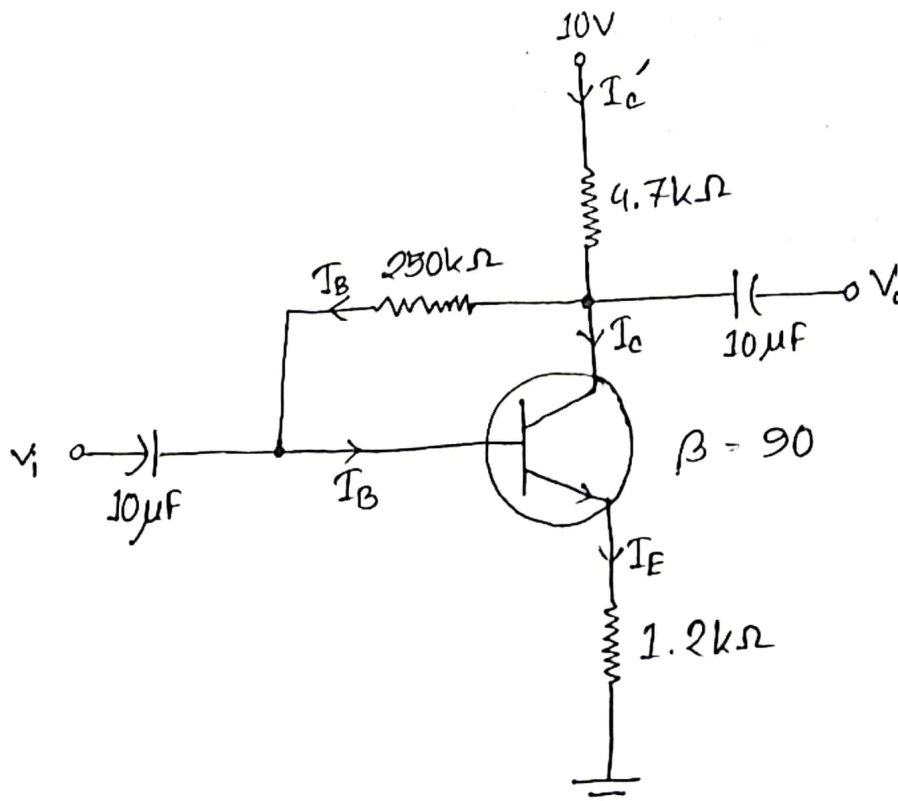

$$\begin{aligned} I_{C'} &= I_C + I_B \\ I_{C'} &= I_C = \beta I_B \\ I_E &= I_C \end{aligned}$$

Applying KVL at input side,

$$-V_{CC} + I_C R_C + I_B R_B + V_{BE} + I_E R_E = 0$$

$$\Rightarrow -V_{CC} + (I_C + I_B) R_C + I_B R_B + V_{BE} + (\beta + 1) I_B R_E = 0$$

$$\Rightarrow -V_{CC} + I_C R_C + I_B R_C + I_B R_B + V_{BE} + (\beta + 1) I_B R_E = 0$$

$$\Rightarrow -V_{CC} + \beta I_B R_C + I_B R_C + I_B R_B + V_{BE} + (\beta + 1) I_B R_E = 0$$

$$\Rightarrow -V_{CC} + I_B (\beta R_C + R_C + R_B + (\beta + 1) R_E) + V_{BE} = 0$$

$$\therefore I_B = \frac{V_{CC} - V_{BE}}{\beta R_C + R_C + R_B + (\beta + 1) R_E}$$

$$= \frac{10 - 0.7}{\cancel{90} R_C (\beta + 1) + R_B + (\beta + 1) R_E}$$

$$= \frac{10 - 0.7}{(\beta + 1)(R_C + R_E) + R_B}$$

$$= \frac{10 - 0.7}{(90 + 1)(4.7 + 1.2) + 250}$$

$$= 0.0118 \text{ mA}$$

$$\therefore I_C = 90 \times 0.0118 = 1.062 \text{ mA}$$

Applying KVL at output side,

$$-V_{CC} + I_C R_C + V_{CE} + I_E R_E = 0$$

$$\Rightarrow -V_{CC} + I_C R_C + V_{CE} + I_C R_E = 0$$


$$\Rightarrow V_{CE} = 10 - I_C (R_C + R_E)$$

$$\therefore V_{CE} = 10 - 1.062(4.7 + 1.2)$$


$$= 3.73 \text{ V}$$

Example:
4.13

Repeat Example 4.12 using a beta of 135.

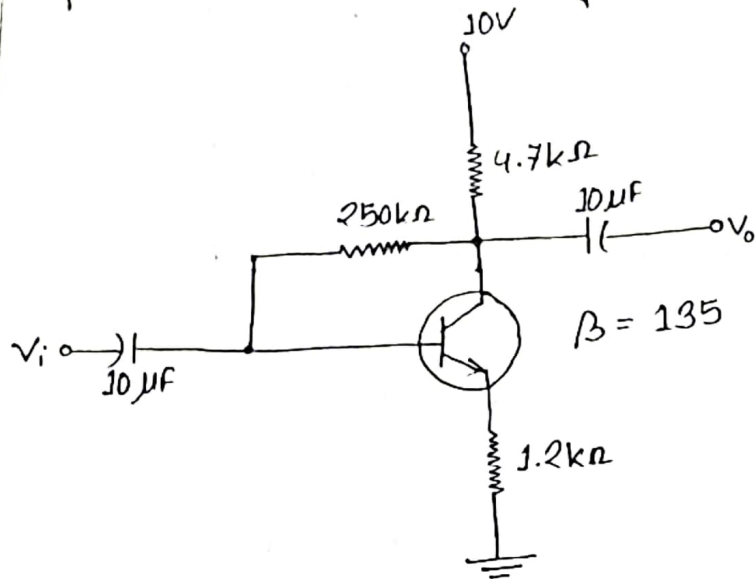

Solution:-

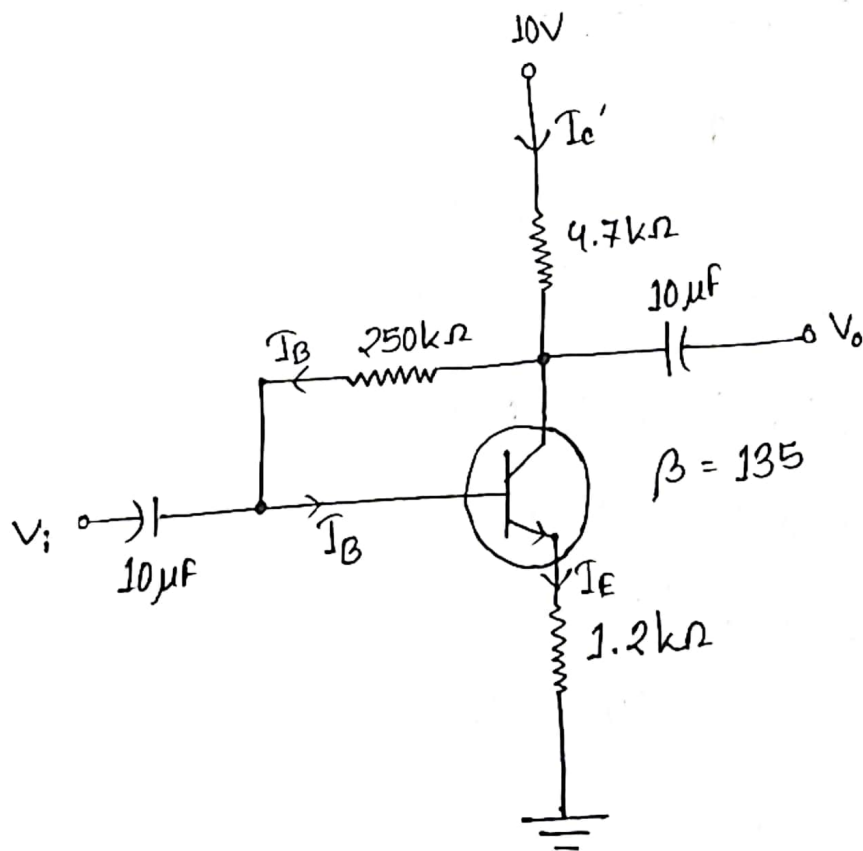

Applying KVL at input side,

$$-V_{CC} + I_C R_C + I_B R_B + V_{BE} + I_E R_E = 0$$

$$\Rightarrow -V_{CC} + (I_C + I_B) R_C + I_B R_B + V_{BE} + (\beta + 1) I_B R_E = 0$$

$$\Rightarrow -V_{CC} + I_C R_C + I_B R_C + I_B R_B + V_{BE} + (\beta + 1) I_B R_E = 0$$

$$\Rightarrow -V_{CC} + \beta I_B R_C + I_B R_C + I_B R_B + V_{BE} + (\beta + 1) I_B R_E = 0$$

$$\Rightarrow -V_{CC} + I_B (\beta R_C + R_C + R_B + (\beta + 1) R_E) + V_{BE} = 0$$

$$\therefore I_B = \frac{V_{CC} - V_{BE}}{\beta R_C + R_C + R_B + (\beta + 1) R_E}$$

$$= \frac{V_{CC} - V_{BE}}{(\beta + 1) R_C + R_B + (\beta + 1) R_E}$$

$$= \frac{V_{CC} - V_{BE}}{(\beta + 1) (R_C + R_E) + R_B}$$

$$= \frac{10 - 0.7}{(135 + 1) (4.7 + 1.2) + 250}$$

$$= 8.836 \mu A$$

$$\therefore I_C = \beta I_B = 135 \times 8.836 = 1192.86 \mu A$$
$$= 1.19 \text{ mA}$$

Applying KVL at output side,

$$-V_{CC} + I_C R_C + V_{CE} + I_E R_E = 0$$

$$\Rightarrow -V_{CC} + I_C R_C + V_{CE} + I_C R_E = 0$$

$$\therefore V_{CE} = V_{CC} - I_C (R_C + R_E)$$


$$= 10 - 1.19 (4.7 + 1.2)$$

$$= 2.979 \text{ V}$$


Example

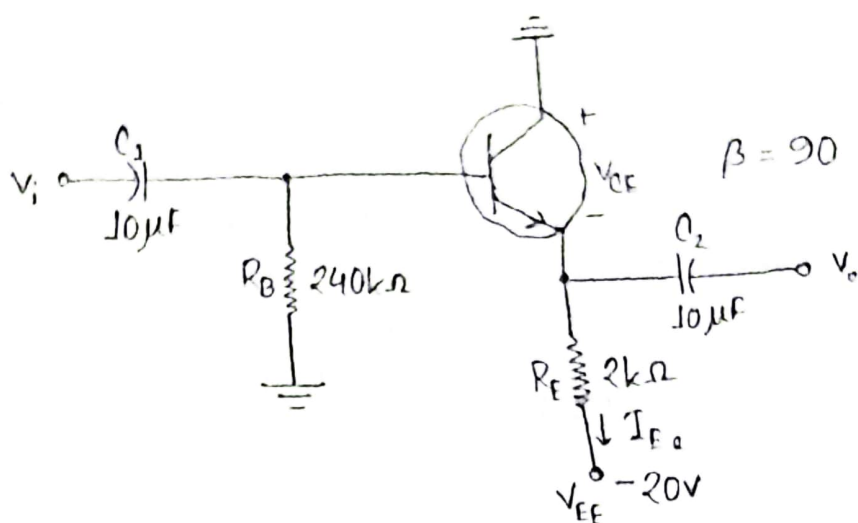4.16

Determine V_{CE} and I_{E0} for the network of figure.



Solution:-

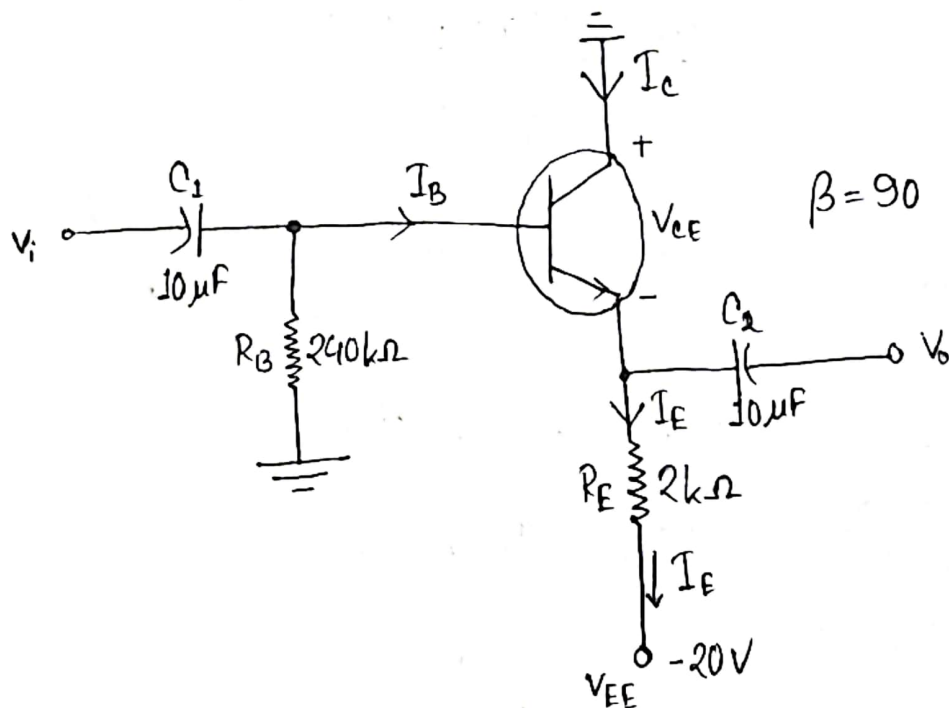

Applying KVL at input side,

$$I_B R_B + V_{BE} + I_E R_E - V_{EE} = 0$$

$$\Rightarrow I_B R_B + V_{BE} + (\beta + 1) I_B R_E - V_{EE} = 0$$

$$\Rightarrow I_B (R_B + (\beta + 1) R_E) = V_{EE} - V_{BE}$$

$$\begin{aligned} \therefore I_B &= \frac{V_{EE} - V_{BE}}{R_B + (\beta + 1) R_E} \\ &= \frac{20 - 0.7}{240 + (90 + 1) \times 2} \\ &= 0.0457 \text{ mA} \end{aligned}$$

$$\begin{aligned} I_E &= (\beta + 1) I_B \\ &= (90 + 1) \times 0.0457 \\ &= 4.16 \text{ mA} \end{aligned}$$

Applying KVL at output side,

$$V_{CE} + I_E R_E - V_{EE} = 0$$


$$\Rightarrow V_{CE} = V_{EE} - I_E R_E$$

$$\begin{aligned} \therefore V_{CE} &= 20 - (4.16 \times 2) \\ &= 11.68 \text{ V} \end{aligned}$$

MOSFET

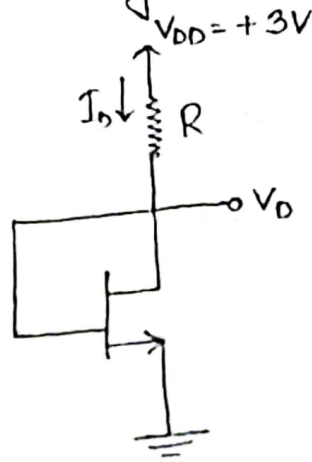Example: 01

In the following NMOS, $I_D = 0.16 \text{ mA}$, $V_t = 0.6 \text{ V}$, $K_n' = 200 \mu\text{A/V}^2$, $L = 0.4 \mu\text{m}$ and $W = 4 \mu\text{m}$. Find the value of R neglecting channel length and modulation effect.



Solution:-

$$V_{GS} = V_G - V_S = V_G$$

$$V_{DS} = V_D - V_S = V_D$$

$$\therefore V_G = V_D$$


$$\therefore V_{DS} \geq V_{GS} - V_T \quad [\text{Saturation mode}]$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$

$$\Rightarrow (V_{GS} - V_T)^2 = \frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}$$

$$\Rightarrow (V_{GS} - V_T)^2 = \frac{2 \times 0.16 \times 10^{-3}}{200 \times 10^{-6} \times \frac{4}{0.4}} = 0.16$$

$$\therefore V_{GS} - V_T = \pm 0.4$$

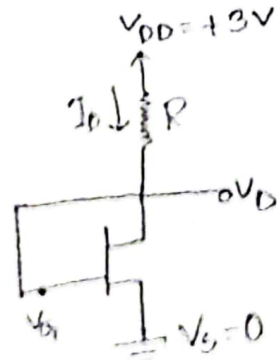

$$I_D = 0.16 \text{ mA} \\ = 0.16 \times 10^{-3} \text{ A}$$

$$V_t = 0.6 \text{ V}$$

$$K_n' = 200 \mu\text{A/V}^2$$

$$L = 0.4 \mu\text{m}$$

$$W = 4 \mu\text{m}$$

$$\begin{aligned} V_{GS} &= 0.4 + V_i \\ &= 0.4 + 0.6 \\ &= 1 \text{ V} \end{aligned}$$

$$\begin{aligned} \therefore V_{DS} &= V_D - V_S \\ \therefore V_{DS} &= V_D = 1 \text{ V} \end{aligned}$$


$$V_{GS} = V_{DS} = 1 \text{ V}$$

$$\therefore R = \frac{V_{DD} - V_D}{I_D} = \frac{3 - 1}{0.16 \times 10^{-3}} = 12500 \Omega = 12.5 \text{ k}\Omega$$

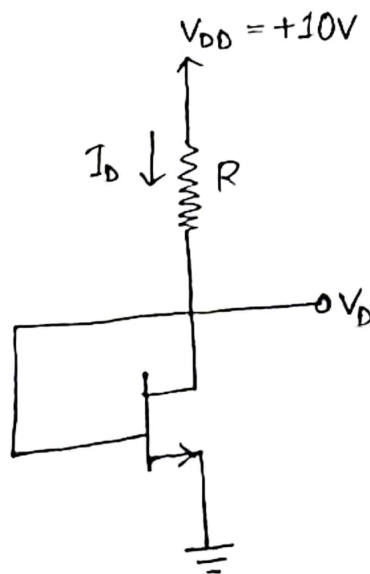Example:

02

In the following NMOS, $I_D = 0.4 \text{ mA}$, $V_t = 2 \text{ V}$, $\mu_n C_{ox} = 20 \text{ } \mu\text{A/V}^2$, $L = 10 \text{ } \mu\text{m}$ and $W = 100 \text{ } \mu\text{m}$. Find the value of R neglecting channel length and modulation effect.



Solution:-

Here,


$$I_D = 0.4 \text{ mA} = 0.4 \times 10^{-3} \text{ A}$$

$$V_i = 2 \text{ V}$$

$$\mu_n C_{ox} = 20 \mu\text{A/V}^2$$

$$L = 10 \mu\text{m}$$

$$W = 100 \mu\text{m}$$

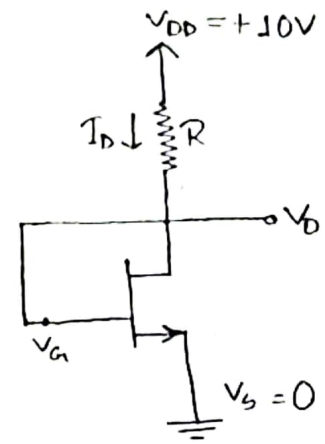

$$V_{GS} = V_G - V_S = V_G$$

$$V_{DS} = V_D - V_S = V_D$$

$$\therefore V_D = V_G$$

$$\therefore V_{DS} \geq V_{GS} - V_T \text{ [Saturation Mode]}$$

$$\therefore I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$

$$\Rightarrow (V_{GS} - V_T)^2 = \frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}$$

$$\Rightarrow (V_{GS} - V_T)^2 = \frac{2 \times 0.4 \times 10^{-3}}{20 \times 10^{-6} \times \frac{100}{10}} = 4$$

$$\therefore V_{GS} - V_T = \pm 2$$

$$\therefore V_{GS} = 2 + V_T = 2 + 2 = 4 \text{ V}$$


$$\therefore V_{DS} = V_{GS} = 4 \text{ V}$$

$$\begin{aligned} \therefore V_{DS} &= V_D - V_S \\ \Rightarrow V_{DS} &= V_D = 4 \text{ V} \end{aligned}$$


$$\therefore R = \frac{V_{DD} - V_D}{I_D} = \frac{10 - 4}{0.4 \times 10^{-3}} = 15000 \Omega = 15 \text{ k}\Omega$$

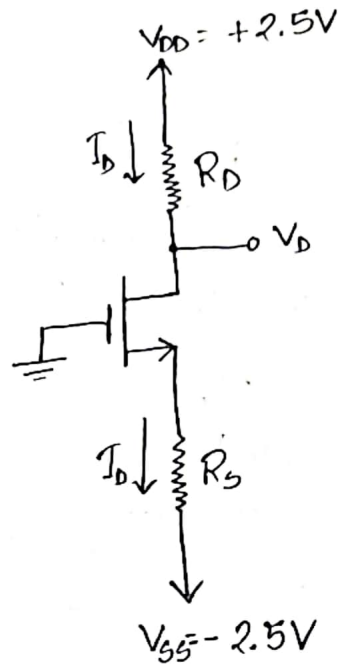Example: 03

Design the circuit of figure, that is, determine the values of R_D and R_S , so that the transistor operates at $I_D = 0.4 \text{ mA}$ and $V_D = +0.5 \text{ V}$. The NMOS transistor has $V_t = 0.7 \text{ V}$, $\mu_n C_{ox} = 100 \mu\text{A/V}^2$, $L = 1 \mu\text{m}$ and $W = 32 \mu\text{m}$. Neglect the channel-length modulation effect.



Solution:-

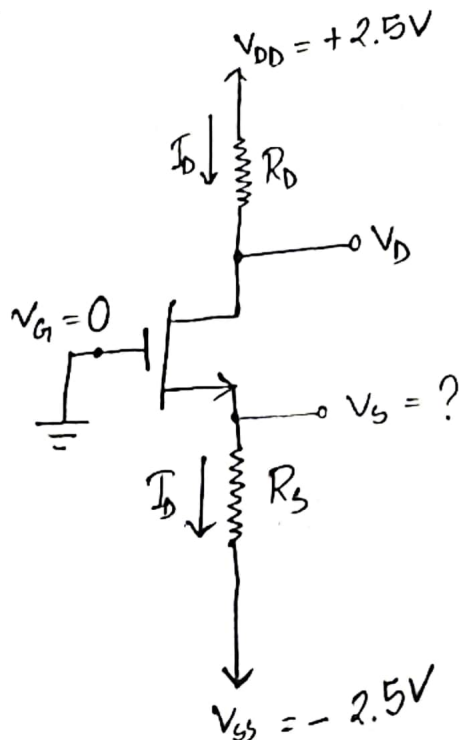

$$\begin{aligned}
 I_D &= 0.4 \text{ mA} \\
 &= 0.4 \times 10^{-3} \text{ A} \\
 V_D &= +0.5 \text{ V} \\
 V_t &= 0.7 \text{ V} \\
 \mu_n C_{ox} &= 100 \mu\text{A/V}^2 \\
 L &= 1 \mu\text{m} \\
 W &= 32 \mu\text{m}
 \end{aligned}$$

$$R_D = \frac{V_{DD} - V_D}{I_D}$$

$$= \frac{2.5 - 0.5}{0.4} = 5k\Omega$$

V_{DS} $\rightarrow V_D - \cancel{V_S}$ $= 0.5$	$V_{GS} - V_T$ $\rightarrow V_G - \cancel{V_S} - V_T$ $= 0 - 0.7$ $= -0.7$
---	---

$V_{DS} > V_{GS} - V_T$ [Saturation Mode]

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$

$$\Rightarrow (V_{GS} - V_T)^2 = \frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}$$

$$\Rightarrow (V_{GS} - V_T)^2 = \frac{2 \times 0.4 \times 10^{-3}}{100 \times 10^{-6} \times \frac{32}{1}} = 0.25$$

$$\therefore V_{GS} - V_T = \pm 0.5$$

$$\therefore V_{GS} = 0.5 + V_T = 0.5 + 0.7 = 1.2V$$

$$V_{GS} = V_G - V_S$$

$$\Rightarrow V_S = V_G - V_{GS} = 0 - 1.2 = -1.2V$$


$$\therefore V_S - I_D R_S = V_{SS}$$

$$\Rightarrow R_S = \frac{V_S - V_{SS}}{I_D}$$


$$\therefore R_S = \frac{-1.2 + 2.5}{0.4} = 3.25k\Omega$$

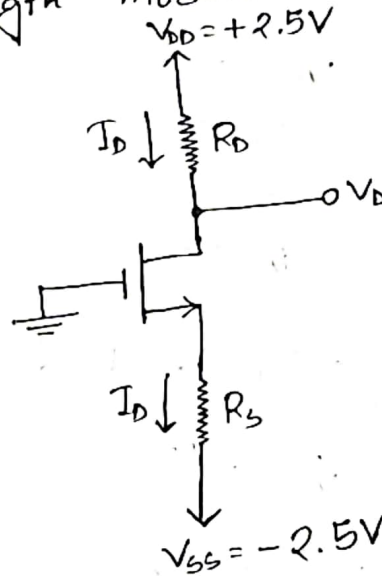Example: 04

A NMOS transistor in the circuit of figure, has $R_D = 5k\Omega$ and $R_S = 3.25k\Omega$. The transistor operates at $I_D = 0.4mA$ and $V_D = +0.5V$. It has $V_t = 0.7V$, $\mu_n C_{ox} = 100 \mu A/V^2$, $L = 1 \mu m$. Determine the value of gate width, W . Neglect the channel-length modulation effect.



Solution:-

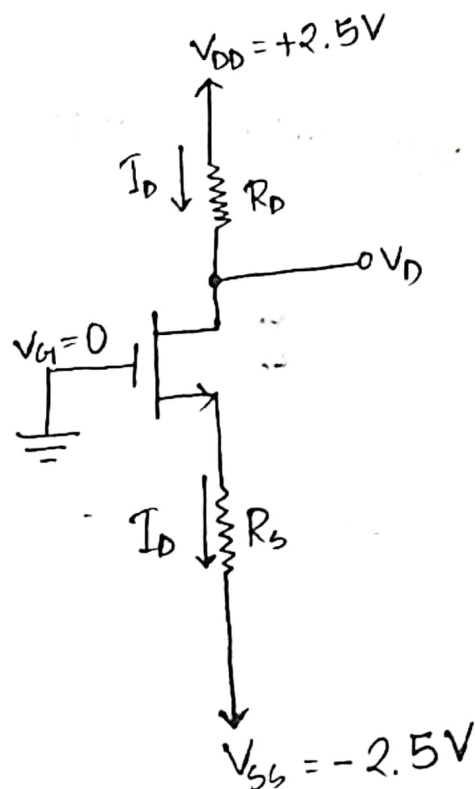

Here,

$$I_D = 0.4 \text{ mA} = 0.4 \times 10^{-3} \text{ A}$$

$$V_D = +0.5 \text{ V}$$

$$V_t = 0.7 \text{ V}$$

$$\mu_n C_{ox} = 100 \mu\text{A/V}^2$$

$$L = 1 \mu\text{m}$$

$$R_D = 5 \text{ k}\Omega$$

$$R_S = 3.25 \text{ k}\Omega$$

$$V_{DS} \\ \Rightarrow V_D - V_S \\ \Rightarrow 0.5$$

$$V_{GS} - V_t \\ \Rightarrow V_G - V_S - V_t \\ \Rightarrow 0 - 0.7 \\ = -0.7$$

$$\therefore V_{DS} > V_{GS} - V_t \text{ [Saturation Mode]}$$

$$\therefore I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$

$$\Rightarrow \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2 = 2I_D$$

$$V_S - I_D R_S = V_{SS}$$

$$\Rightarrow V_S = V_{SS} + I_D R_S$$

$$\Rightarrow V_S = -2.5 + (0.4 \times 10^{-3}) \times (3.25 \times 10^3)$$

$$\therefore V_S = -1.2 \text{ V}$$

$$V_{GS} = V_G - V_S$$

$$= 0 - (-1.2) = 1.2 \text{ V}$$

Now,

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$

$$\Rightarrow \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2 = 2I_D$$

$$\Rightarrow \frac{W}{L} (V_{GS} - V_T)^2 = \frac{2I_D}{\mu_n C_{ox}}$$


$$\Rightarrow W = \frac{2I_D L}{\mu_n C_{ox} (V_{GS} - V_T)^2}$$

$$\Rightarrow W = \frac{2 \times 0.4 \times 10^{-3} \times 1 \times 10^{-6}}{100 \times 10^{-6} \times (1.2 - 0.7)^2}$$


$$\therefore W = 3.2 \times 10^{-5} \text{ m} = 32 \mu\text{m} \quad (\text{Ans!})$$

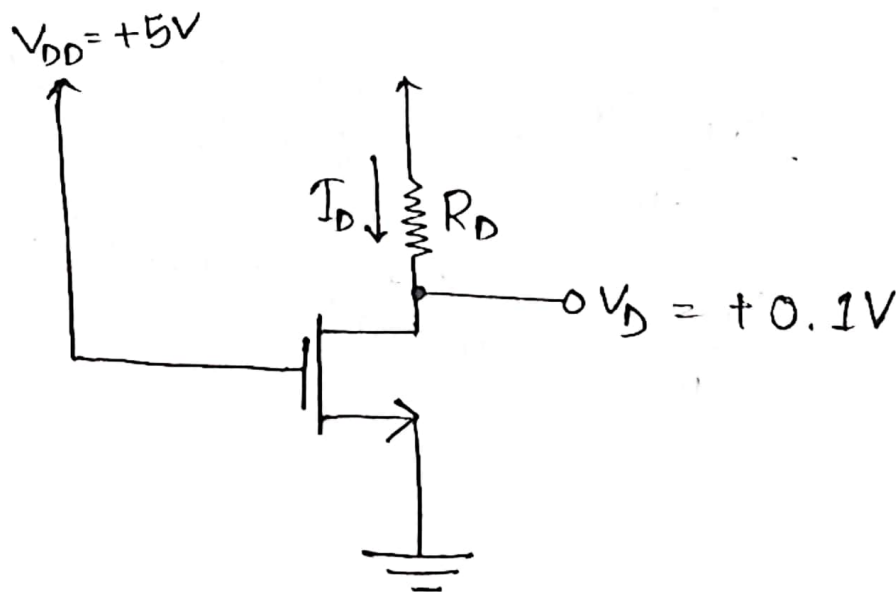Example:
05

Design the circuit in figure, to establish a drain voltage of 0.1V. What is the effective resistance between drain and source at this operating point? Let $V_T = 1\text{V}$ and $k_n'(W/L) = 1 \text{ mA/V}^2$.



Solution:-

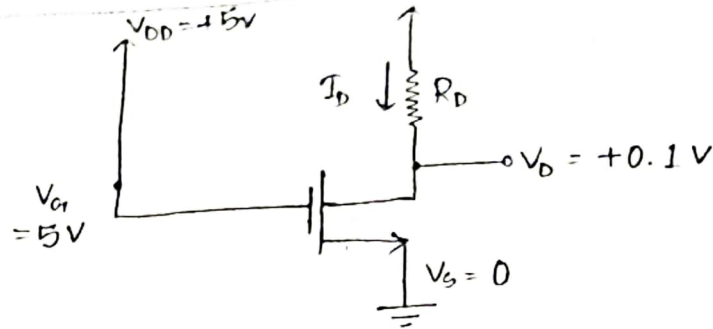

$$V_t = 1V; k_n' (W/L) = 1mA/V^2$$

$$V_{DS} = V_D - V_S$$

$$= 0.1 - 0$$

$$= 0.1$$

$$V_{GS} - V_T$$

$$= V_G - V_S - V_T$$

$$= 5 - 1$$

$$= 4$$

$$V_{DS} < V_{GS} - V_T \quad [\text{Triode Mode}]$$

$$I_D = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_T) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$$= 1 \times 10^{-3} \left[(5-1) \times 0.1 - \frac{1}{2} (0.1)^2 \right]$$

$$= 3.95 \times 10^{-4} = 0.395 \text{ mA}$$


$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{5 - 0.1}{0.395} = 12.4 \text{ k}\Omega$$

$$R_{DS} = \frac{V_{DS}}{I_D} = \frac{0.1}{0.395} = 0.25 \text{ k}\Omega$$

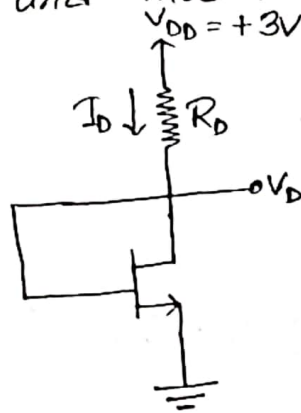Example:

06

Design the circuit in figure to obtain a current I_D of $80 \mu A$. Find the value required for R and find the dc voltage V_D . Let the NMOS transistor have $V_t = 0.6 V$, $\mu_n C_{ox} = 200 \mu A/V^2$, $L = 0.8 \mu m$ and $W = 4 \mu m$. Neglect the channel length and modulation effect.



Solution:-

Here,

$$I_D = 80 \mu A = 80 \times 10^{-6} A$$

$$V_t = 0.6 V$$

$$\mu_n C_{ox} = 200 \mu A/V^2$$

$$L = 0.8 \mu m$$


$$W = 4 \mu m$$

$$V_{DS} = V_D - V_S = V_D$$

$$V_{GS} = V_G - V_S = V_G$$

$$V_{DD} = V_G$$
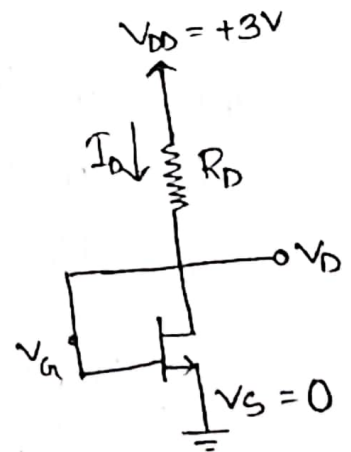
$$\therefore V_{DS} \geq V_{GS} - V_t \quad [\text{Saturation Mode}]$$



$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$

$$\Rightarrow (V_{GS} - V_T)^2 = \frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}$$

$$\Rightarrow (V_{GS} - V_T)^2 = \frac{2 \times 80 \times 10^{-6}}{200 \times 10^{-6} \times \frac{4}{0.8}}$$

$$\Rightarrow (V_{GS} - V_T)^2 = 0.16$$

$$\therefore V_{GS} - V_T = \pm 0.4$$

$$\therefore V_{GS} = 0.4 + V_T = 0.4 + 0.6 = 1V$$

$$\therefore V_{GS} = V_{DS} = 1V$$

$$V_{DS} = V_D - V_S$$

$$\Rightarrow V_D = V_{DS} + V_S = 1 + 0 = 1V$$

$$\therefore V_D = 1V$$


$$R = \frac{V_{DD} - V_D}{I_D}$$

$$= \frac{3 - 1}{80 \times 10^{-6}} = 25000 \Omega = 25k\Omega$$

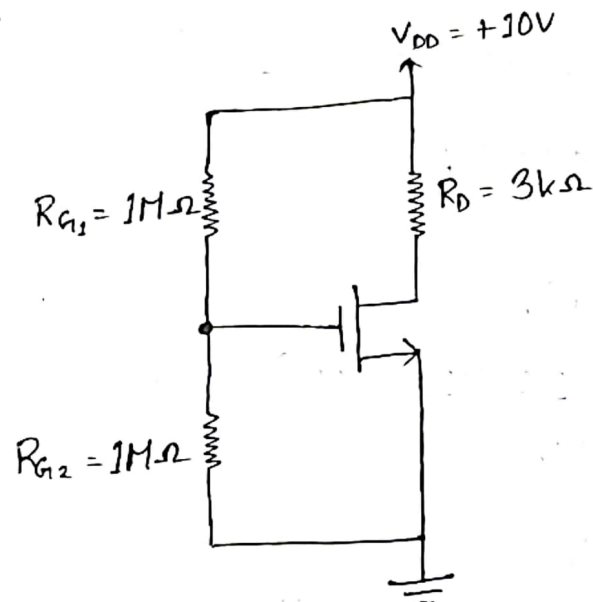
Example:

07

Find I_{Dmax} that can flow through the ideal N-MOSFET. Also find V_{DS} at I_{Dmax} . Given $V_{th} = 1.5V$ and $K_n'(W/L) = 2.76 \times 10^{-6} A/V^2$. Find the power dissipated in the MOSFET.



Solution:-

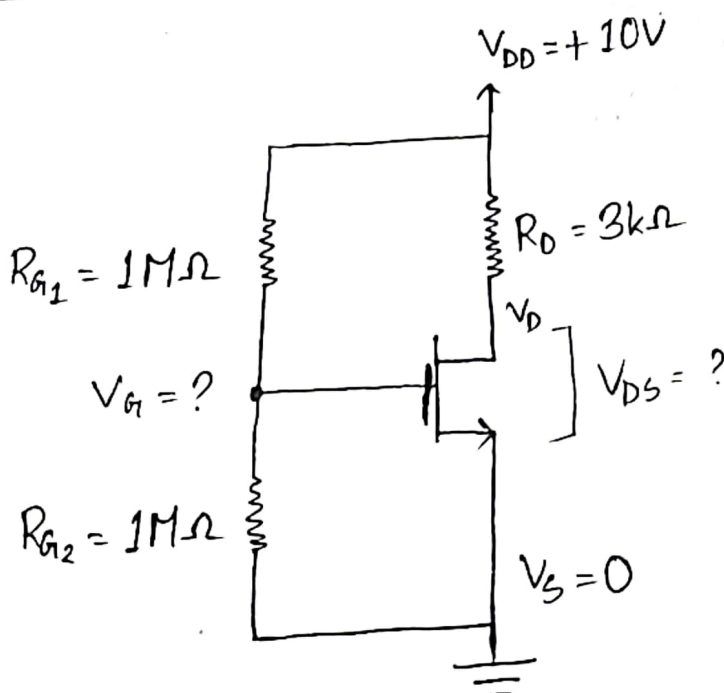

$$V_{G_s} = \frac{R_{G_s}}{R_{G_s} + R_{G_d}} \times V_{DD}$$

$$= \frac{1}{1+1} \times 10 = 5V$$

$$V_{GS} = V_{G_s} - V_{S_s}$$

$$= 5 - 0 = 5V$$

Let's assume the MOSFET in Saturation Mode,

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})^2$$

$$= \frac{1}{2} \times 2.76 \times 10^{-6} \times (5 - 1.5)^2$$

$$= 1.69 \times 10^{-5} A$$

$$\therefore V_D = V_{DD} - I_D R_D$$

$$= 10 - (1.69 \times 10^{-5} \times 3)$$

$$= 9.99V$$

$$\therefore V_{DS} = V_D - V_{S_s}$$

$$= 9.99 - 0 = 9.99V$$


$$P_D = V_{DS} I_D$$

$$= 9.99 \times 1.69 \times 10^{-5}$$

$$= 1.68 \times 10^{-4} W$$

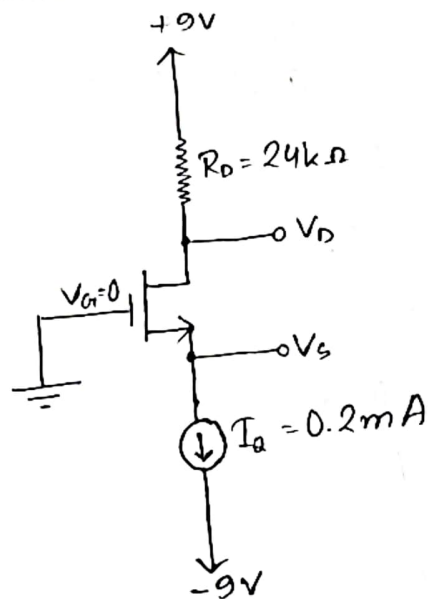Example:
08

In the following NMOS Transistor $V_t = 0.6\text{ V}$ and $K_n'(W/L) = 200\text{ }\mu\text{A/V}^2$. Determine the value of V_s and V_D .



Solution:-

$$\begin{aligned} V_D &= 9 - I_D R_D \\ &= 9 - (0.2 \times 10^{-3} \times 24 \times 10^3) \\ &= 4.2\text{ V} \end{aligned}$$

$$\begin{array}{l|l} V_{DS} & V_{GS} - V_T \\ V_D - V_s & V_G - V_s - V_T \\ = 4.2 & 0 - 0.6 \\ & - - 0.6 \end{array}$$

$\therefore V_{DS} > V_{GS} - V_T$ [Saturation Mode]

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$

$$\Rightarrow (V_{GS} - V_T)^2 = \frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}$$

$$\Rightarrow (V_{GS} - V_T)^2 = \frac{2 \times 0.2 \times 10^{-3}}{200 \times 10^{-6}}$$

$$\Rightarrow (V_{GS} - V_T)^2 = 2$$

$$\therefore V_{GS} - V_T = \pm 1.41$$

$$\therefore V_{GS} = 1.41 + V_T$$

$$= 1.41 + 0.6$$

$$= 2.01 \text{ V}$$

$$\therefore V_{GS} = V_G - V_S$$


$$\Rightarrow V_S = V_G - V_{GS}$$

$$\therefore V_S = 0 - 2.01$$

$$= -2.01 \text{ V}$$

OP-AMP

Example: 5.3

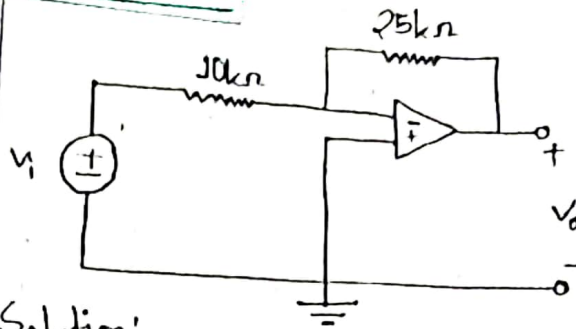

Refer to the op amp in figure.
If $V_i = 0.5V$, calculate (a) the output voltage V_o , and (b) the current in the $10k\Omega$ resistor.


Solution:-

$$(a) V_o = -\frac{R_f}{R_i} \times V_i$$

$$= -\frac{25}{10} \times 0.5 = -1.25V$$

$$(b) i = \frac{V_i - 0}{R_i} = \frac{0.5 - 0}{10 \times 10^3} = 50\mu A$$

Practice Problem: 5.3

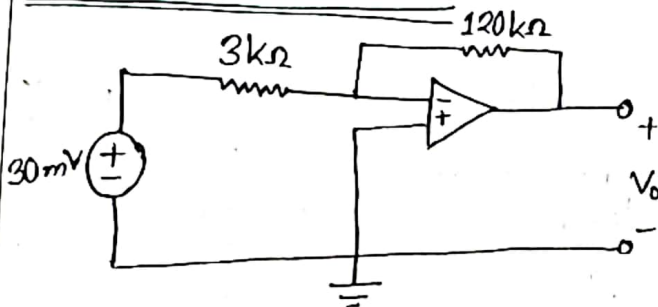

Find the output of the op amp circuit shown in figure. Calculate the current through the feedback resistor.

Solution:-

$$V_o = -\frac{R_f}{R_i} \times V_i$$

$$= -\frac{120}{3} \times 30$$


$$= -1200mV$$

$$= -1.2V$$

$$i = \frac{0 - V_o}{R_f}$$
$$= \frac{0 - (-1.2)}{120 \times 10^3}$$
$$= 10\mu A$$

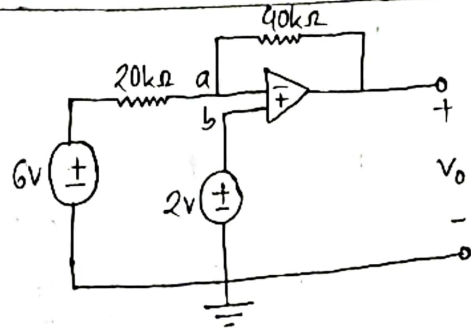Example: 5.4

Determine V_o in the op amp circuit shown in figure.



Solution:-

Applying KCL at node a,


$$\frac{V_i - V_a}{R_i} = \frac{V_a - V_o}{R_f}$$

$$\Rightarrow \frac{6 - 2}{20} = \frac{2 - V_o}{40}$$

$$\Rightarrow 160 = 40 - 20V_o$$

$$\Rightarrow -20V_o = 120$$

$$\therefore V_o = -6V$$

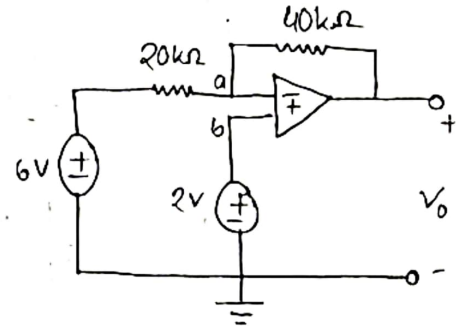

Practice Problem: 5.4



Two kinds of current-to-voltage converters (also known as transresistance amplifiers) are shown in figure.

(a) Show that for the converter in figure (a),

$$\frac{V_o}{i_s} = -R$$

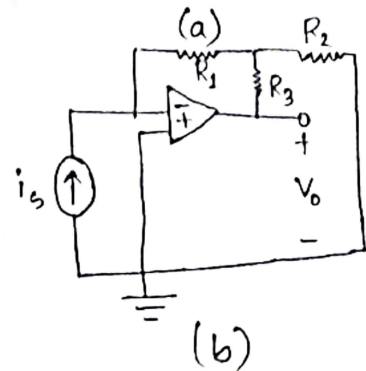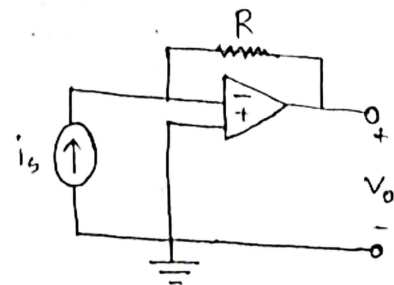(b) Show that for the converter in figure (b);

$$\frac{V_o}{i_s} = -R_1 \left(1 + \frac{R_3}{R_1} + \frac{R_3}{R_2} \right)$$



Solution:-


(a) Applying KCL at node a,

$$i_s = \frac{V_a - V_o}{R}$$

$$\Rightarrow i_s = \frac{0 - V_o}{R}$$

$$\Rightarrow -R = \frac{V_o}{i_s}$$
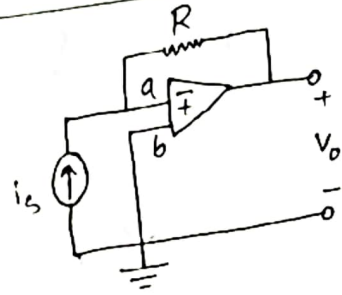
$$\therefore \frac{V_o}{i_s} = -R \text{ (showed)}$$




(b) Applying KCL at node A,

$$i_s = 0 + \frac{V_A - V_B}{R_1}$$

$$\Rightarrow i_s = \frac{0 - V_B}{R_1}$$

$$\Rightarrow i_s = -\frac{V_B}{R_1}$$

$$\therefore V_B = -i_s R_1$$

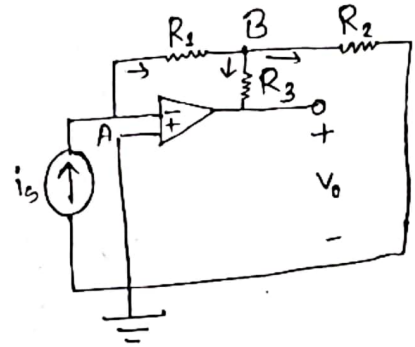

Applying KCL at node B,

$$\frac{V_A - V_B}{R_1} = \frac{V_B - V_o}{R_3} + \frac{V_B - 0}{R_2}$$

$$\Rightarrow \frac{i_s R_1}{R_1} = \frac{-i_s R_1 - V_o}{R_3} + \frac{-i_s R_1}{R_2}$$

$$\Rightarrow \frac{i_s R_1}{R_1} = -\frac{i_s R_1}{R_3} - \frac{V_o}{R_3} - \frac{i_s R_1}{R_2}$$

$$\Rightarrow \frac{V_o}{R_3} = -i_s - \frac{i_s R_1}{R_3} - \frac{i_s R_1}{R_2}$$


$$\Rightarrow V_o = -i_s R_3 - i_s R_1 - \frac{i_s R_1 R_3}{R_2}$$

$$\Rightarrow \frac{V_o}{i_s} = -R_3 - R_1 - \frac{R_1 R_3}{R_2}$$

$$\Rightarrow \frac{V_o}{i_s} = -R_1 \left(\frac{R_3}{R_1} + 1 + \frac{R_3}{R_2} \right)$$

$$\therefore \frac{V_o}{i_s} = -R_1 \left(1 + \frac{R_3}{R_1} + \frac{R_3}{R_2} \right) \text{ (showed)}$$

Example: 5.5

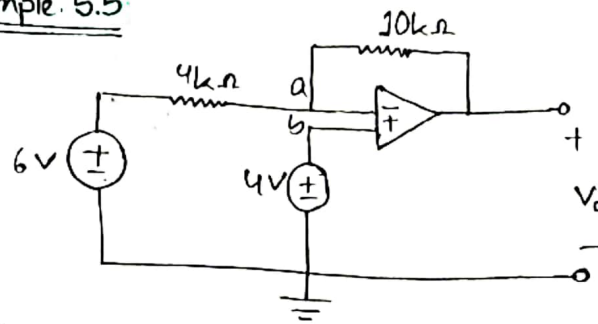

For the op amp circuit in figure, calculate the output voltage V_o .

Solution:-

Applying KCL at node a,

$$\frac{V_i - V_a}{R_1} = \frac{V_a - V_o}{R_f}$$


$$\Rightarrow \frac{6 - 4}{4} = \frac{4 - V_o}{10}$$

$$\Rightarrow 20 = 16 - 4V_o$$

$$\Rightarrow -4V_o = 4$$

$$\therefore V_o = -1V \quad (\underline{\text{Ans}})$$

Example: 5.6

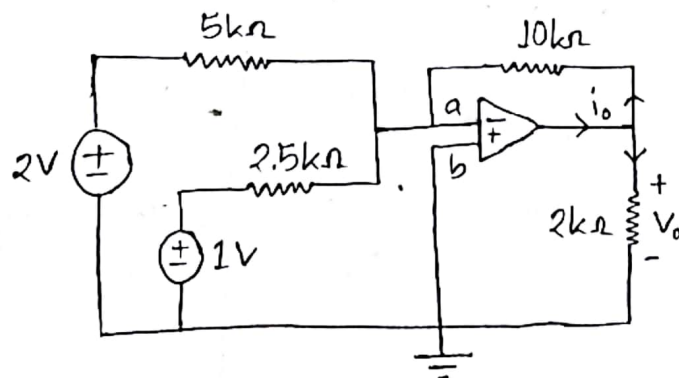

Calculate V_o and i_o in the op amp circuit in figure

Solution:-

Applying KCL at node a,

or

$$V_o' = -\frac{10}{5} \times 2 = -4V$$

$$V_o'' = -\frac{10}{2.5} \times 1 = -4V$$


$$\therefore V_o = V_o' + V_o'' = -4 - 4 = -8V$$

Applying KCL at output,


$$i_o = I_1 + I_2$$

$$= \frac{V_o - 0}{10} + \frac{V_o - 0}{2}$$
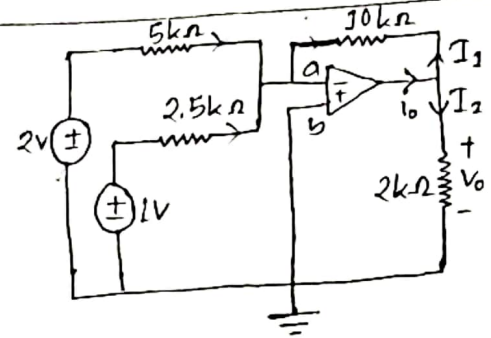
$$= \frac{-8}{10} + \frac{-8}{2} = -4.8mA$$



Practice Problem: 5.6

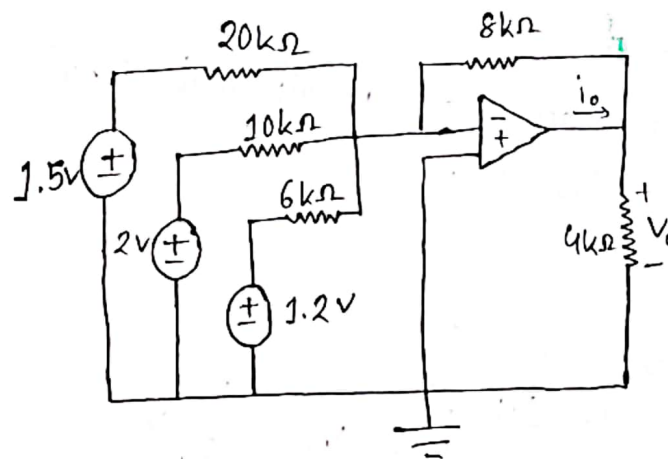

find V_o and i_o in the op amp circuit shown in figure.

Solution:-

$$V_0' = -\frac{8}{20} \times 1.5$$

$$= -0.6 \text{ V}$$

$$V_0'' = -\frac{8}{10} \times 2$$

$$= -1.6 \text{ V}$$

$$V_0''' = -\frac{8}{6} \times 1.2 = -1.6 \text{ V}$$


$$\therefore V_0 = -0.6 - 1.6 - 1.6 = -3.8 \text{ V}$$

Applying KCL at output,

$$i_0 = I_1 + I_2$$

$$= \frac{V_0 - 0}{8} + \frac{V_0 - 0}{4}$$
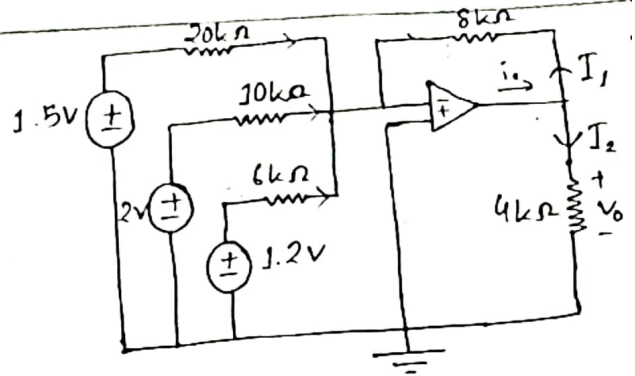
$$= \frac{-3.8}{8} + \frac{-3.8}{4} = -1.425 \text{ mA}$$



Example: 5.7

Design an op amp circuit with inputs V_1 and V_2 such that $V_0 = -5V_1 + 3V_2$.

Solution:-

$$V_0 = 3V_2 - 5V_1$$

$$\therefore V_0 = \frac{R_2 \left(1 + \frac{R_1}{R_2}\right)}{R_1 \left(1 + \frac{R_3}{R_4}\right)} V_2 - \frac{R_2}{R_1} V_1$$

Here,

$$\frac{R_2}{R_1} = 5 \quad \left| \quad \frac{R_1}{R_2} = \frac{1}{5} \right.$$

$$\Rightarrow R_2 = 5R_1$$

Now,

$$\frac{R_2 \left(1 + \frac{R_3}{R_4}\right)}{R_1 \left(1 + \frac{R_3}{R_4}\right)} = 3$$

$$\Rightarrow \frac{5 \left(1 + \frac{1}{5}\right)}{\left(1 + \frac{R_3}{R_4}\right)} = 3$$

$$\Rightarrow \frac{6}{\frac{R_4 + R_3}{R_4}} = 3 \Rightarrow \frac{6}{1 + \frac{R_3}{R_4}} = 3$$


$$\Rightarrow 6 = 3 \left(1 + \frac{R_3}{R_4}\right)$$

$$\Rightarrow 2 = 1 + \frac{R_3}{R_4}$$

$$\therefore R_3 = R_4$$

Example: 6.13

If $v_1 = 10 \cos 2t$ mV and $v_2 = 0.5t$ mV, find v_o in the op amp circuit in figure. Assume that the voltage across the capacitor is initially zero.

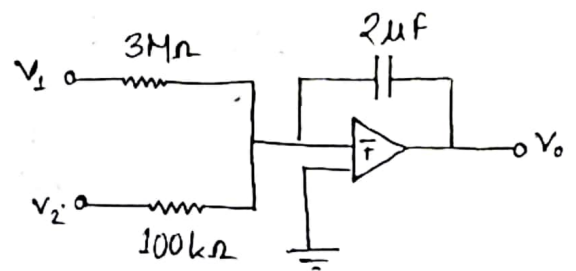Solution:-

Here,

$$v_1 = 10 \cos 2t \text{ mV}$$

$$v_2 = 0.5t \text{ mV}$$

$$v_o' = - \frac{1}{R_1 C} \int v_1 dt$$

$$= - \frac{1}{3 \times 10^6 \times 2 \times 10^{-6}} \int_0^t 10 \cos 2t dt$$

$$= - \frac{1}{6} \times \frac{10 \sin 2t}{2}$$


$$= - 0.833 \sin 2t$$

$$\begin{aligned}
 V_o'' &= - \frac{1}{R_2 C} \int V_2 dt \\
 &= - \frac{1}{100 \times 10^3 \times 2 \times 10^{-6}} \int_0^t 0.5t dt \\
 &= - 5 \cdot \frac{0.5t^2}{2} \\
 &= - 1.25 t^2
 \end{aligned}$$

$$\begin{aligned}
 \therefore V_o &= V_o' + V_o'' \\
 &= - 0.833 \sin 2t - 1.25 t^2 \text{ mV}
 \end{aligned}$$

Practice Problem: 6.13

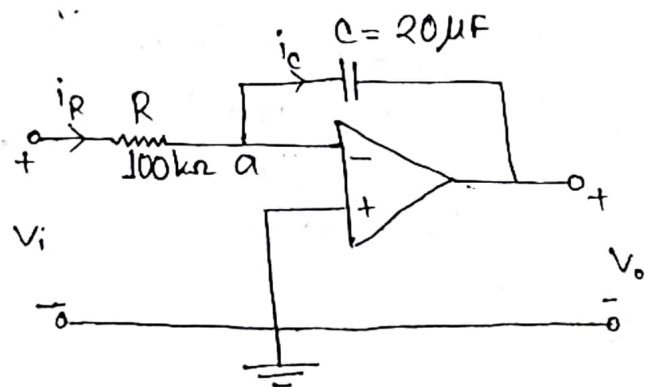The integrator in figure has $R = 100 \text{ k}\Omega$, $C = 20 \mu\text{F}$. Determine the output voltage when a dc voltage of 10 mV is applied at $t = 0$. Assume that the op amp is initially nulled.




Solution:-

$$\begin{aligned}
 V_o &= - \frac{1}{RC} \int V_i dt \\
 &= - \frac{1}{100 \times 10^3 \times 20 \times 10^{-6}} \int_0^t 10 dt \\
 &= - \frac{10}{2} [t]_0^t \\
 &= - 5t \text{ mV}
 \end{aligned}$$

~~Example~~Practice Problem: 6.14

The differentiation in figure has $R = 100\text{ k}\Omega$ and $C = 0.1\text{ }\mu\text{F}$.
 Given that $v_i = 3t\text{ V}$, determine the output v_o .

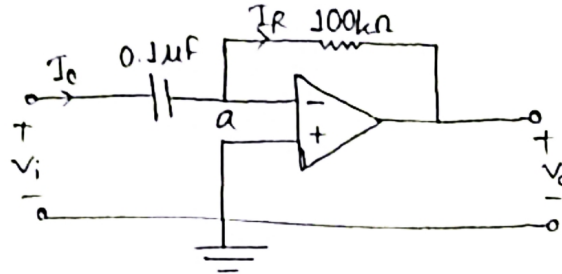Solution:-

$$v_o = -RC \frac{dv_i}{dt}$$

$$= -100 \times 10^3 \times 0.1 \times 10^{-6} \times \frac{d}{dt}(3t)$$

$$= -100 \times 10^3 \times 0.1 \times 10^{-6} \times 3$$

$$= -0.03\text{ V}$$

$$= -30\text{ mV}$$

(Ans:)